```
_____
    -- Block code: sync n edgeDetector.vhd
    -- History: 15.Nov.2017 - 1st version (dqtm)
 3
                  15.Jan.2018 - adapt reset value for usage in mini-project (dqtm)
 4
                  01.Mar.2018 - rename in English (dqtm)
 5
                    <date> - <changes> (<author>)
6
7
    -- Function: edge detector with rise & fall outputs.
    -- Declaring FFs as a shift-register.
8
9
    _____
10
11
    LIBRARY ieee;
12
    USE ieee.std_logic_1164.all;
13
14
   ENTITY sync_n_edgeDetector IS
15
    PORT( data_in : IN std_logic;
          clock : IN std_logic;
reset_n : IN std_logic;
data_sync : OUT std_logic;
16
17
18
           rise : OUT std_logic;
19
           fall
20
                     : OUT std_logic
21
           );
   END sync_n_edgeDetector;
22
2.3
24
25 ARCHITECTURE rtl OF sync_n_edgeDetector IS
        -- Signals & Constants Declaration
2.6
        SIGNAL shiftreg, next_shiftreg: std_logic_vector(2 downto 0);
27
28
29 BEGIN
3.0
31
        -- Process for combinatorial logic
32
        -- OBs.: small logic, could be outside process,
        -- but doing inside for didactical purposes!
33
       _____
34
35
       comb_proc : PROCESS(data_in, shiftreg)
36
       BEGIN
37
           next_shiftreg <= data_in & shiftreg(2 downto 1); -- shift direction
           towards LSB
38
   END PROCESS comb_proc;
39
40
41
       -- Process for registers (flip-flops)
42
       _____
43
       reg_proc : PROCESS(clock, reset_n)
44
       BEGIN
45
           IF reset_n = '0' THEN
              shiftreg <= (OTHERS => '1');
46
47
           ELSIF (rising_edge(clock)) THEN
48
              shiftreg <= next_shiftreg;</pre>
49
           END IF;
      END PROCESS reg_proc;
50
51
52
53
        -- Concurrent Assignments
54
       -- OBs.: no logic after the 1st-FF (shiftreg(2)) because it was added for sync
       purposes
55
        _____
               <= shiftreg(1) AND NOT(shiftreg(0));</pre>
56
       rise
57
                  <= NOT(shiftreg(1)) AND shiftreg(0);
        data_sync <= shiftreg(1); -- take serial_in at same period as</pre>
58
       fall/rise pulse
59
60
   END rtl;
```

61